

Build isolated power supply using capacitors

By Chris Cokayne and Ben Wolde,
Maxim Integrated Products Inc.

Isolated power is usually generated with a transformer, but it can also be generated using capacitors. For some systems, the constraints of size and cost may favour capacitors.

In **Figure 1**, the IC (MAX256) is an integrated primary-side controller and H-bridge driver for isolated power-supply circuits.

Its oscillator, protection circuitry, and internal FET drivers usually provide up to 3W of power to the primary winding of a transformer. In this case, the device drives a pair of capacitors that substitute for the transformer in providing isolation and power transfer.

The IC's adjustable switching frequency (100 kHz to 1 MHz) allows the use of small isolation capacitors, as illustrated below by an equation giving the capacitor impedance at 1 MHz. Losses are negligible at low output power:

$$X_c = 1/(2\pi fC) \\ = 1/(2 \cdot 3.14 \times 10^6 \cdot 0.45 \times 10^{-6}) \approx 0.35 \Omega$$

Complementary square-wave drive signals from the IC (ST₁ and ST₂) are coupled by the isolation capacitors and full-wave rectified by the diodes to produce an isolated output voltage. The high switching frequency also allows use of a small output capacitor. Ignoring switching losses, the output voltage is:

$$V_{out} = V_{in} - 2V_{cap} - 2V_{diode}, \text{ where } V_{cap} = I_{out} \cdot X_c \\ \text{Assuming } I_{out} = 500 \text{ mA, then } V_{out} = 5 - 2(0.5 \cdot 0.35) - 2(0.5) = 5 - 0.35 - 1 \approx 3.7 \text{ V.}$$

This circuit suits applications for which the potential difference across the isolation barrier is fixed. (Capacitors provide

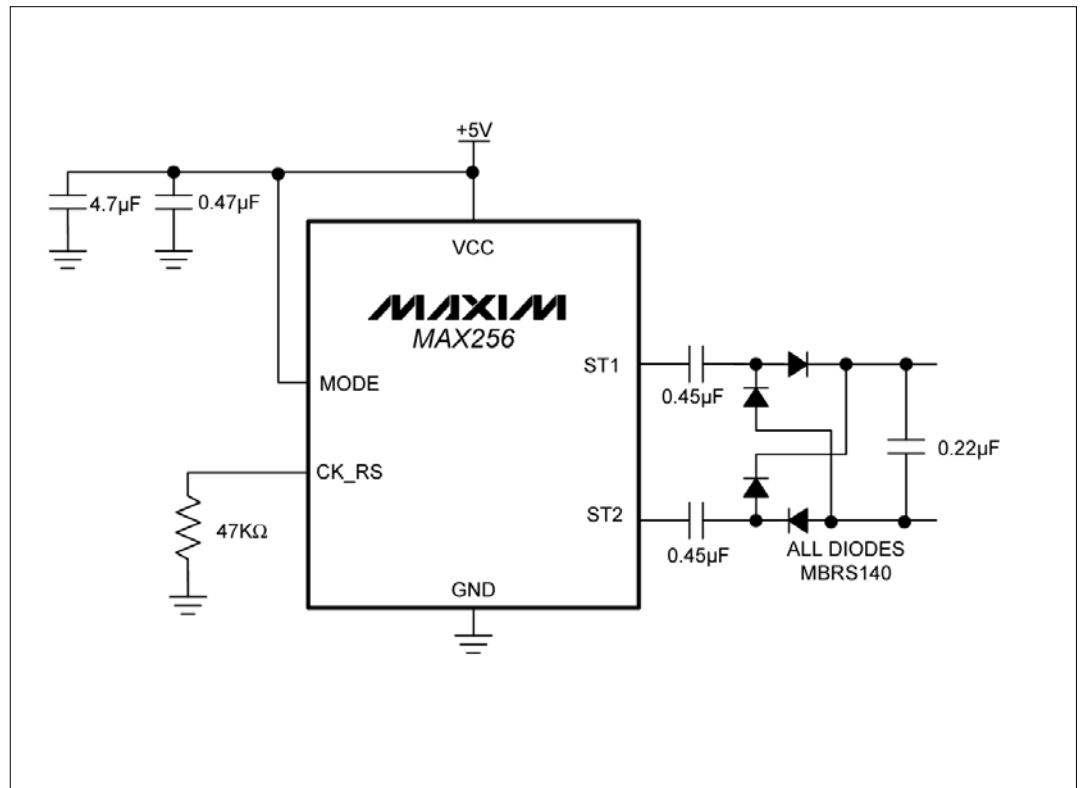


Figure 1: This simple circuit generates a capacitively isolated output voltage.

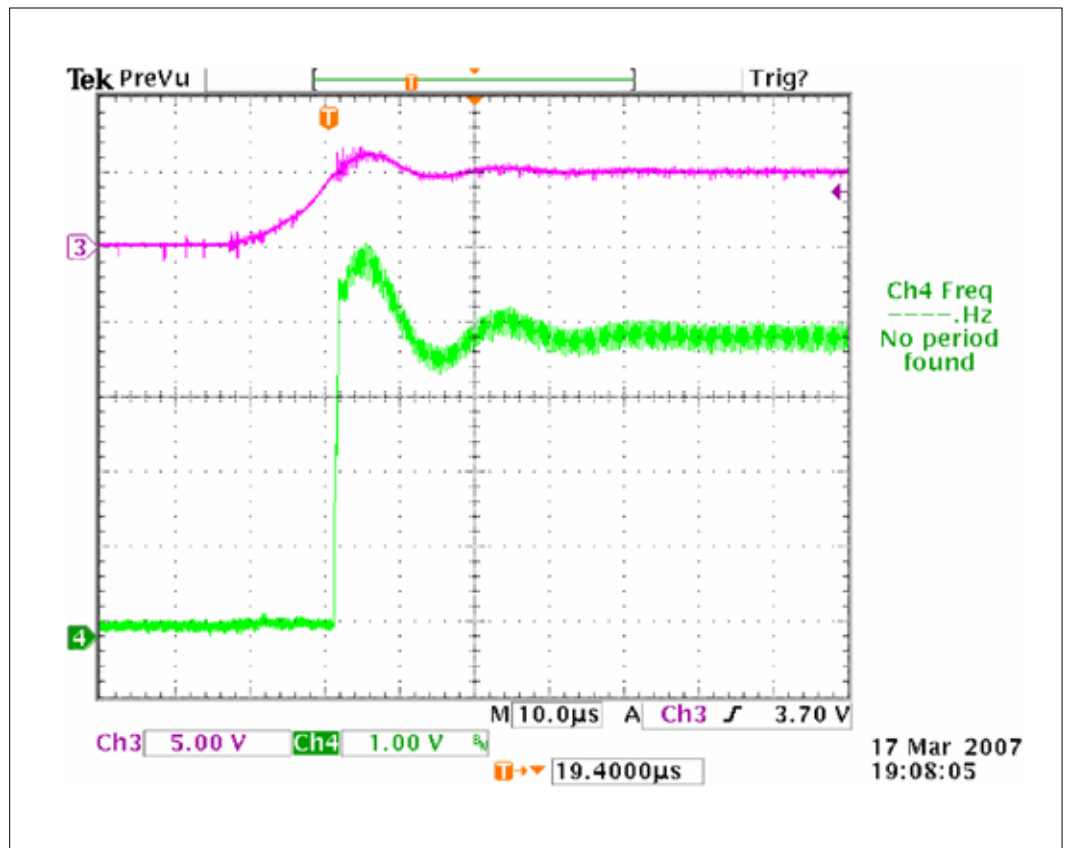


Figure 2: Power-up response of the circuit of Figure 1 with 8-Ω load

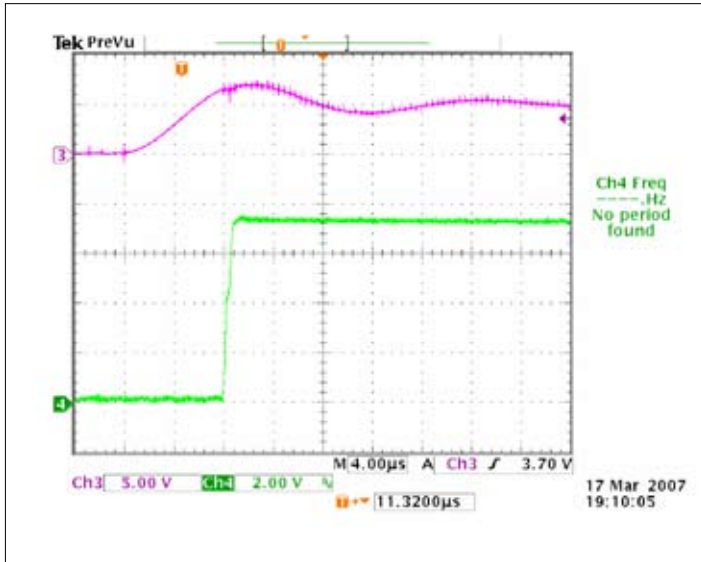


Figure 3: Power-up response of the Figure 1 circuit with no load.

isolation at dc, but not for ac signals.) With the component values shown and a 500 mA load, ripple voltage is about 10% of the dc output level.

You can reduce this ripple

by increasing the value of the output capacitor. Other circuit performance includes the power-up response with 8 Ω (~0.5 A) load (**Figure 2**), the no-load power-up response (**Figure 3**),

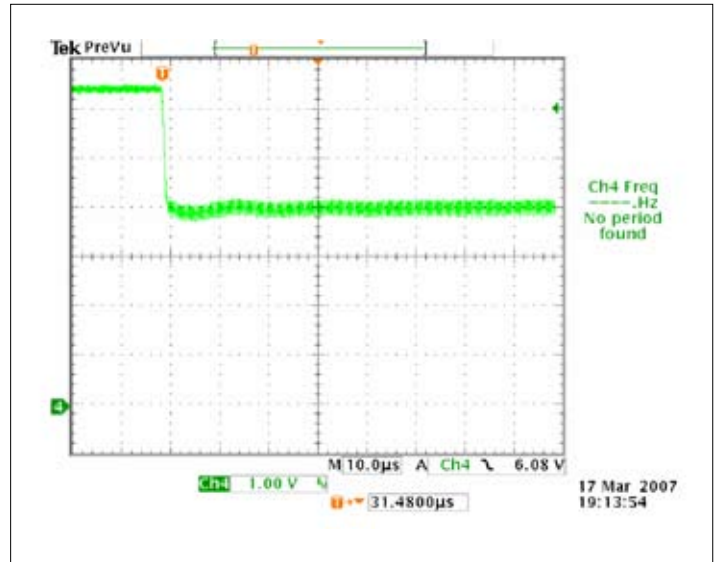


Figure 4: Load-transient response of the Figure 1 circuit, switching from no load to 8- Ω load

and the load-transient response obtained by connecting 8 Ω to an unloaded output (**Figure 4**). In the figures, Channel 3 is the +5 V supply (V_{CC}), and Channel

4 is the voltage across the output capacitor.

[Email](#) [Send inquiry](#)